

Name: \_\_\_\_\_ Ebagnisev Sahiv LopezBorja \_\_\_\_\_


## EEE 202 Lab 6 Data Sheet

### AC Analysis


#### **Part 1 (15 pts): Prelab Calculations and LTSpice Simulation Work**
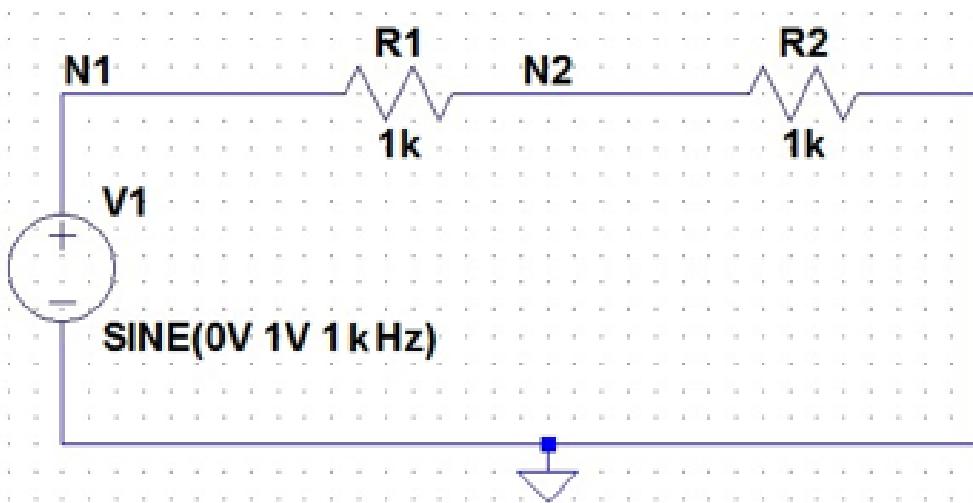
##### **Question 1 – Resistive Circuits**

Build this circuit in LTspice and run a Transient Analysis (.tran) for 10ms:




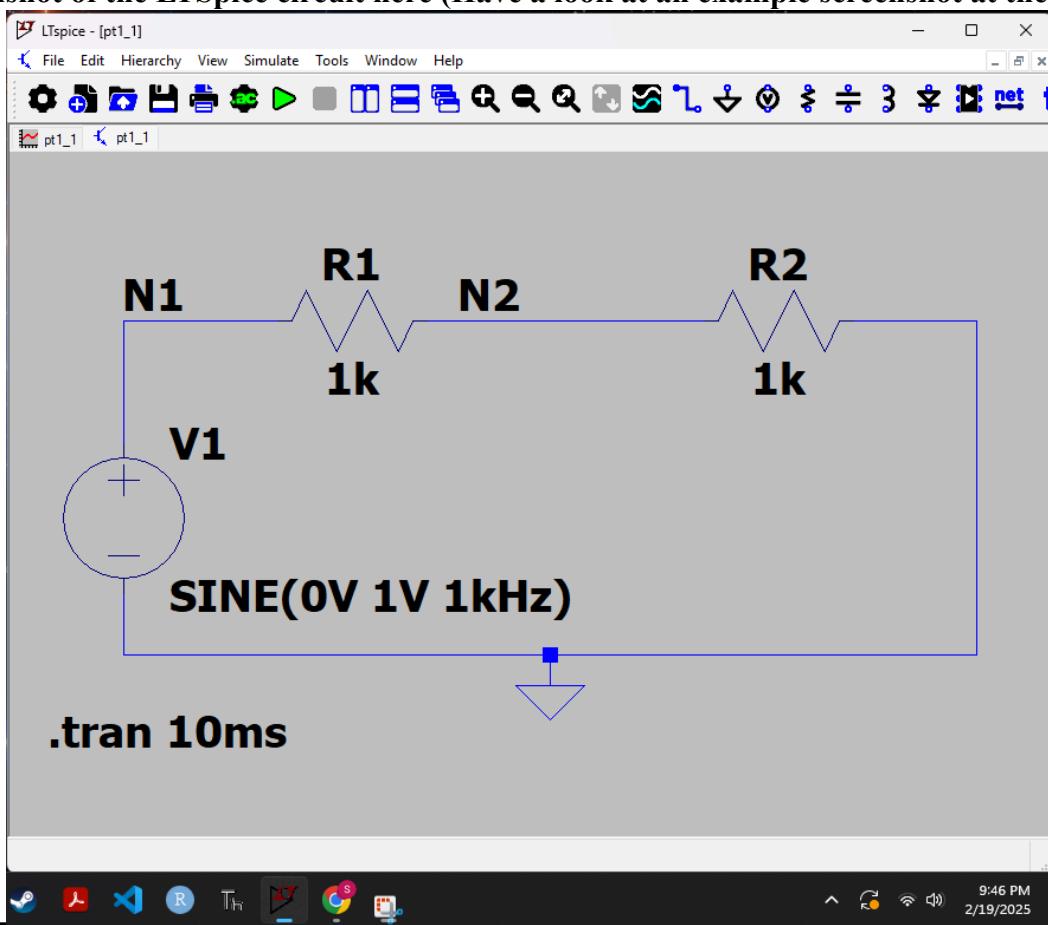Include a screenshot of the LTSpice circuit here (Have a look at an example screenshot at the end of this document):



Simulate in LTspice. Plot the voltage across R1 (N1-N2) and the current (left to right). Make sure the voltage and current curves are plotted on the same plot.

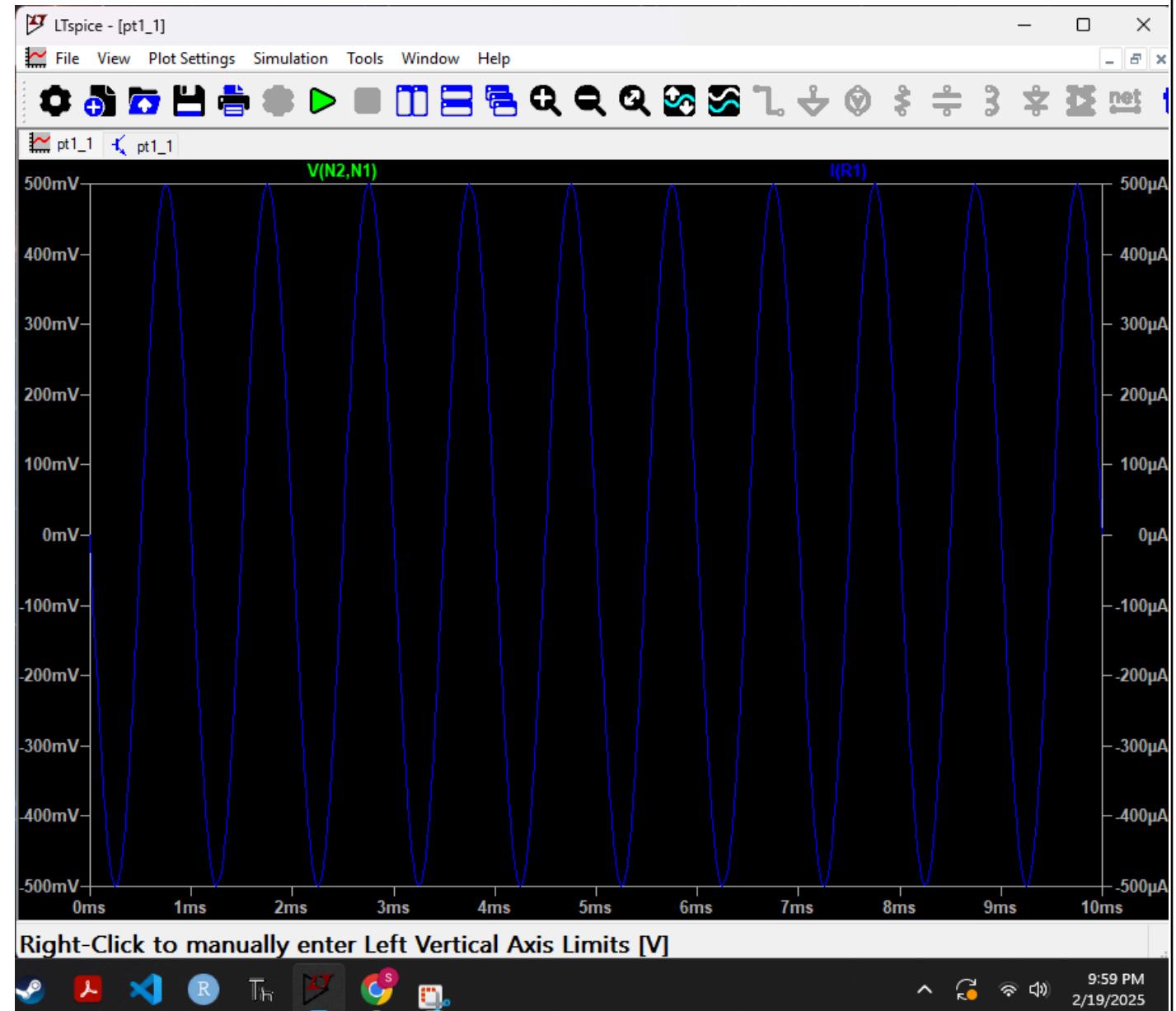Screenshot of LTSpice Plot - Make sure that your computer's date and time are showing up in your screenshot:



Is the current in-phase or out-of-phase with the voltage? Why do you think this is the case?

The current and voltage are in phase. This is the case because our circuit only has resistors and this keeps it in phase.

**Question 2 (RC – Pulse Source):****a) What is the expression for the current,  $i(t)$ :**

Show your steps.

**Steps (handwritten or typed):**

$$V_i(0) = 0V$$

$$V_c(0-) = V_c(0+)$$

$$i(0+) = 1V / 100 \text{ Ohms} = 0.01 \text{ A}$$

$$i(t) = K_1 + K_2 e^{-t/\tau}$$

$$0.01 \text{ A} = K_1 + K_2 \text{ so we have } i(t) = 0.01 e^{-t/\tau}$$

$$\tau = R_{\text{thev}} * C$$

$$i(t) = 0.01 e^{-t/0.00001}$$

**b) What are the expressions for the voltages across the resistor,  $v_R(t)$  and the capacitor,  $v_C(t)$ :**

Show your work.


**Steps (handwritten or typed):**

$$v_R(t) = i(t) * R = e^{-t/0.00001}$$

$$v_C(t) = V_{\text{in}} - v_R(t) = 1 - e^{-t/0.00001}$$

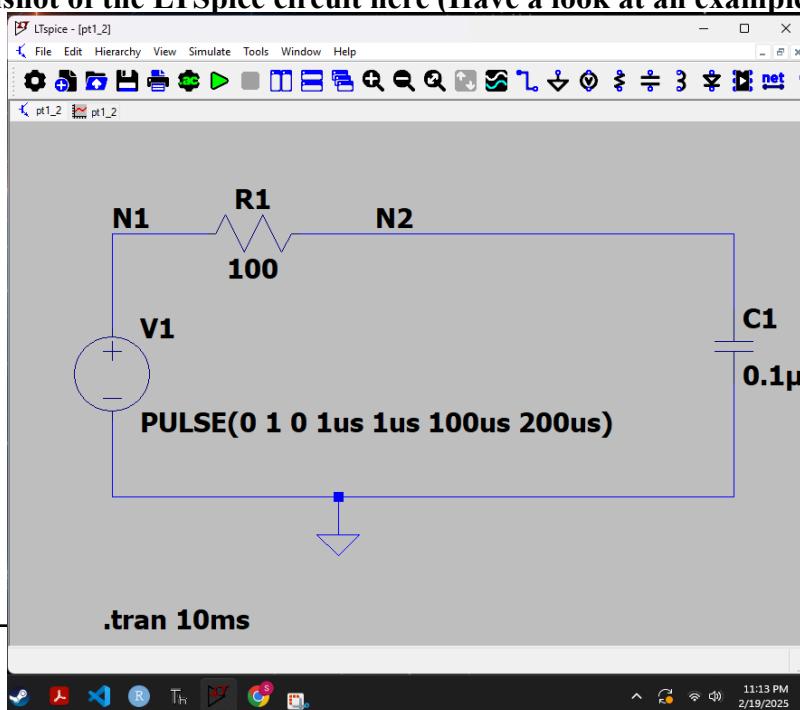
**c) Create a simulation of your RC circuit in LTSpice.**

Include a screenshot of the LTSpice circuit here (Have a look at an example screenshot at the end of this document):



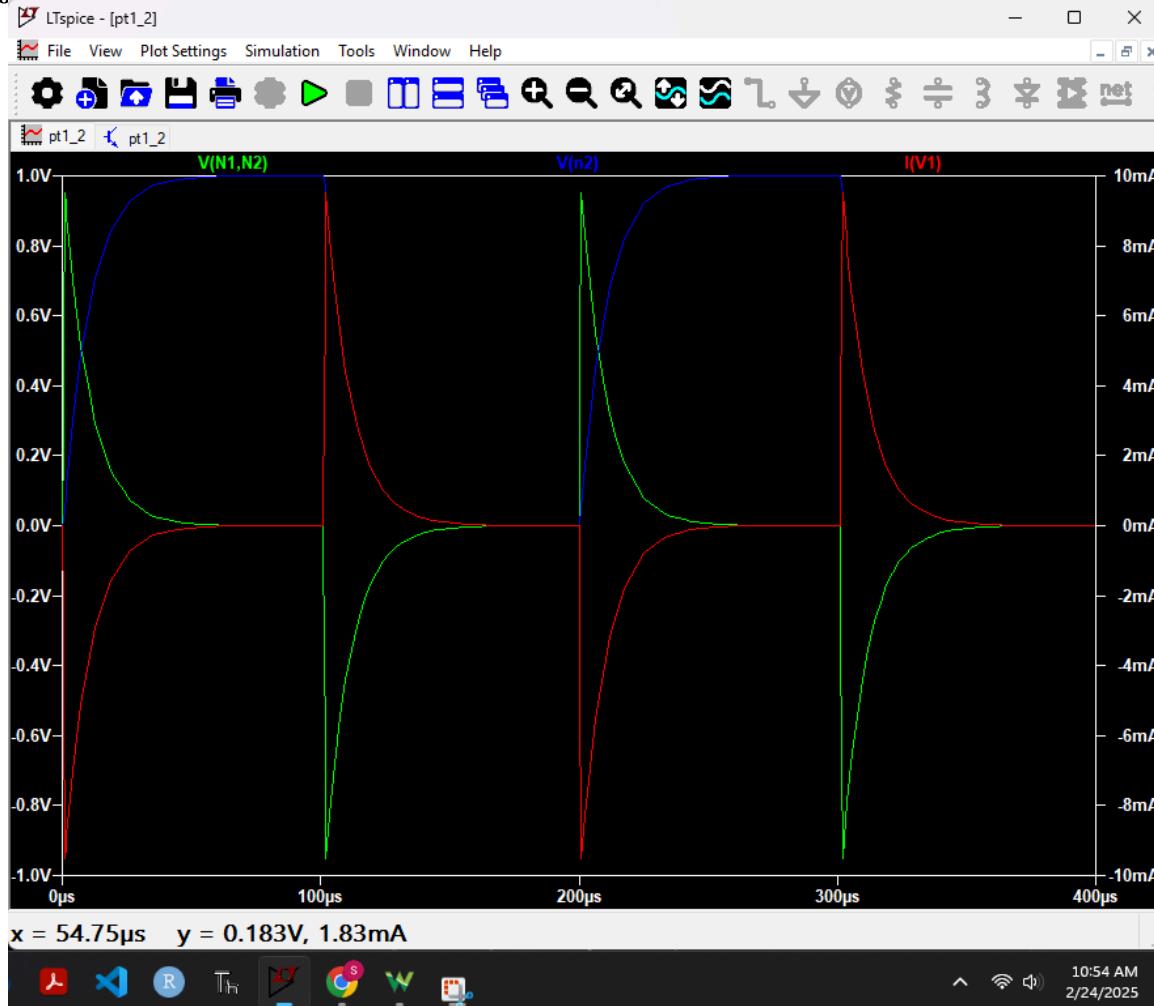d) Create plots of your RC circuit in LTSpice ( $i(t)$ ,  $v_R(t)$ , and  $v_c(t)$  all on the same plot)


Screenshot of LTSpice Plot - Make sure that your computer's date and time are showing up in your:



e) Repeat the LTSpice simulations you carried out in question 1 but with tON, rise time, fall time, and the period all reduced by a factor of 10.

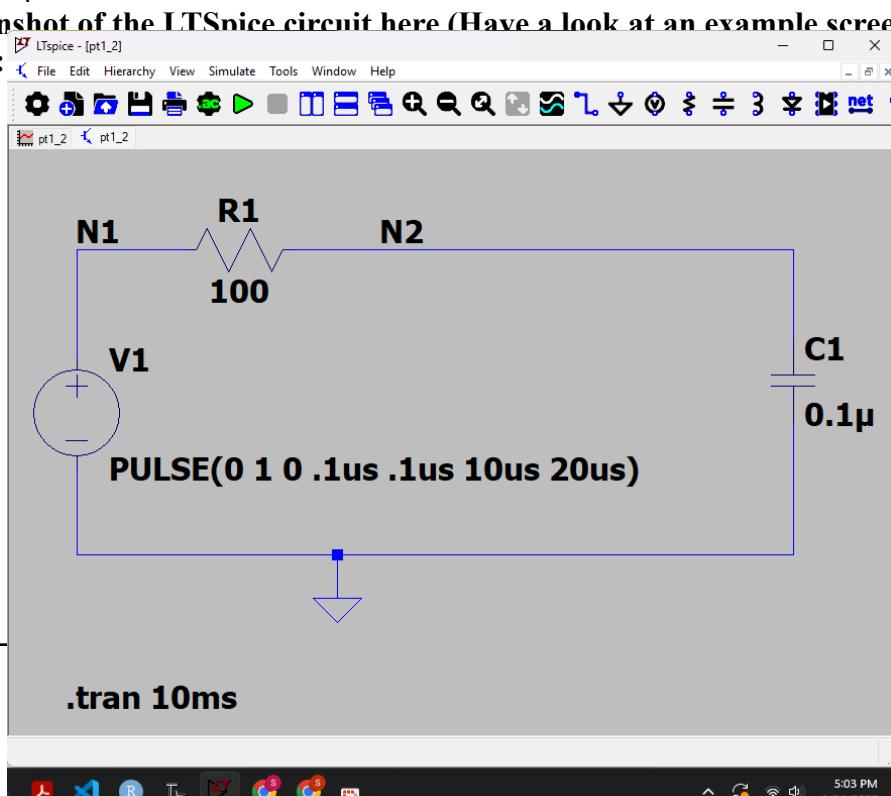
a) LTSpice circuit schematic screenshot

Include a screenshot of the LTSpice circuit here (Have a look at an example screenshot at the end of this document):



- b) Include the plot of  $i(t)$ ,  $v_R(t)$ , and  $v_C(t)$  (all on the same plot).


Screenshot of LTSpice Plot - Make sure that your computer's date and time are showing up in your screenshot:

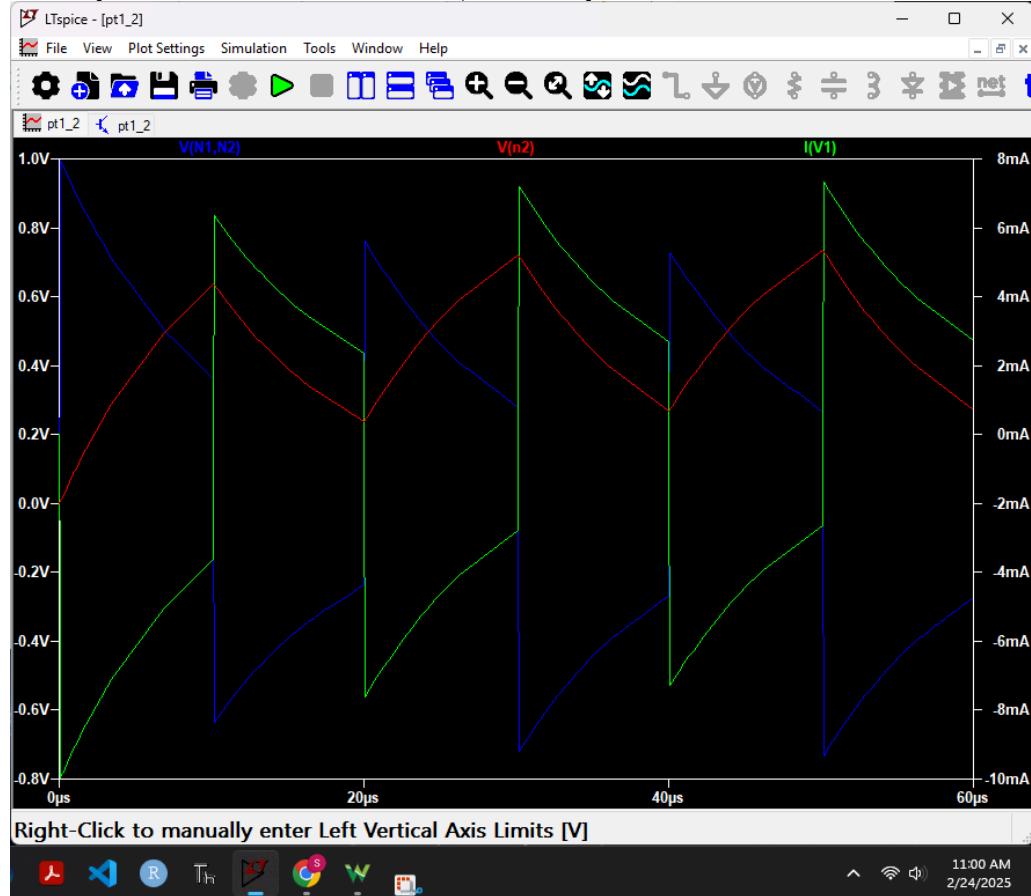


**Question 3 – RC – Sinusoids):**

- a) Create a simulation of your RC circuit and plots of ( $v_s(t)$ ,  $v_R(t)$ , and  $v_c(t)$ ) in LTSPICE and attach the images of your schematic and plots here. *Plot 3 curves on the same plot with 3 cycles each.*

Screenshot of schematic:

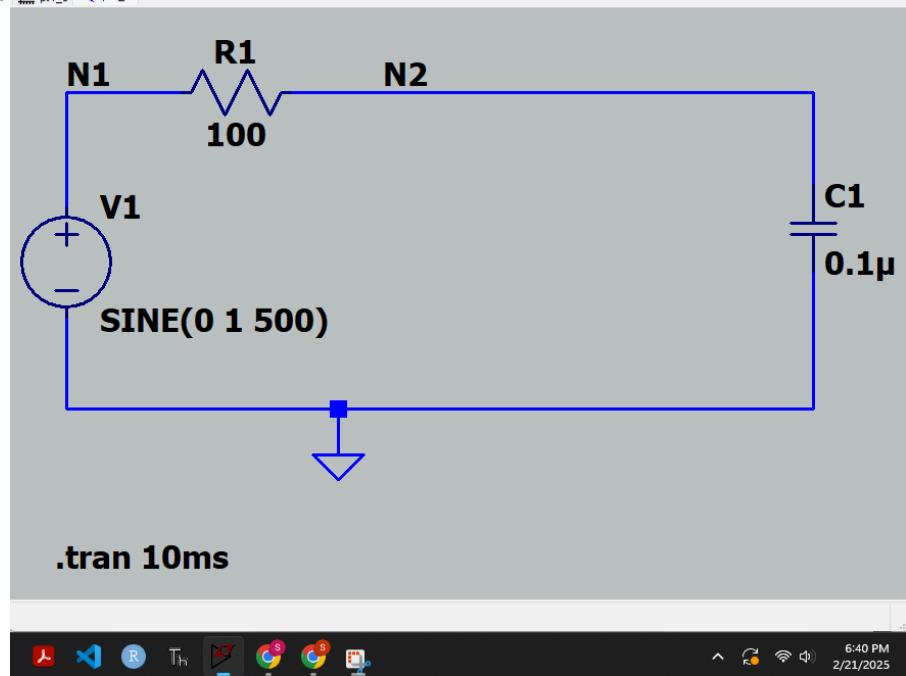

Screenshot of plot:

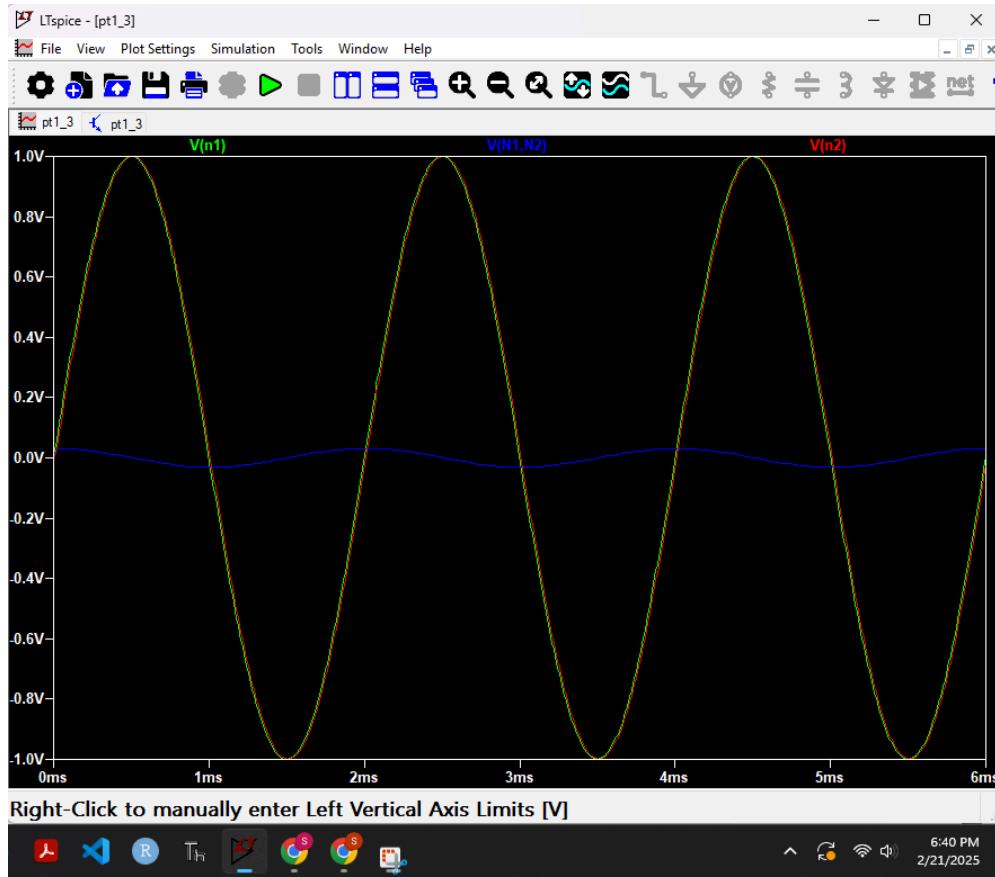


b) Magnitude difference between  $v_s(t)$  and  $v_c(t)$  = 0.5 mV

Phase difference between  $v_s(t)$  and  $v_c(t)$  = 1.98 Degrees  
 $(\Delta t = 511.05 - 500.05)$


#### Question 4 – RL Circuits – Sinusoidal Source:

- a) Create a simulation of your RL circuit and plots of ( $v_s(t)$ ,  $v_R(t)$ , and  $v_L(t)$ ) in LTSPICE and attach the images of your schematic and plots here. *Plot 3 curves on the same plot with 3 cycles each.*

Screenshot of schematic:

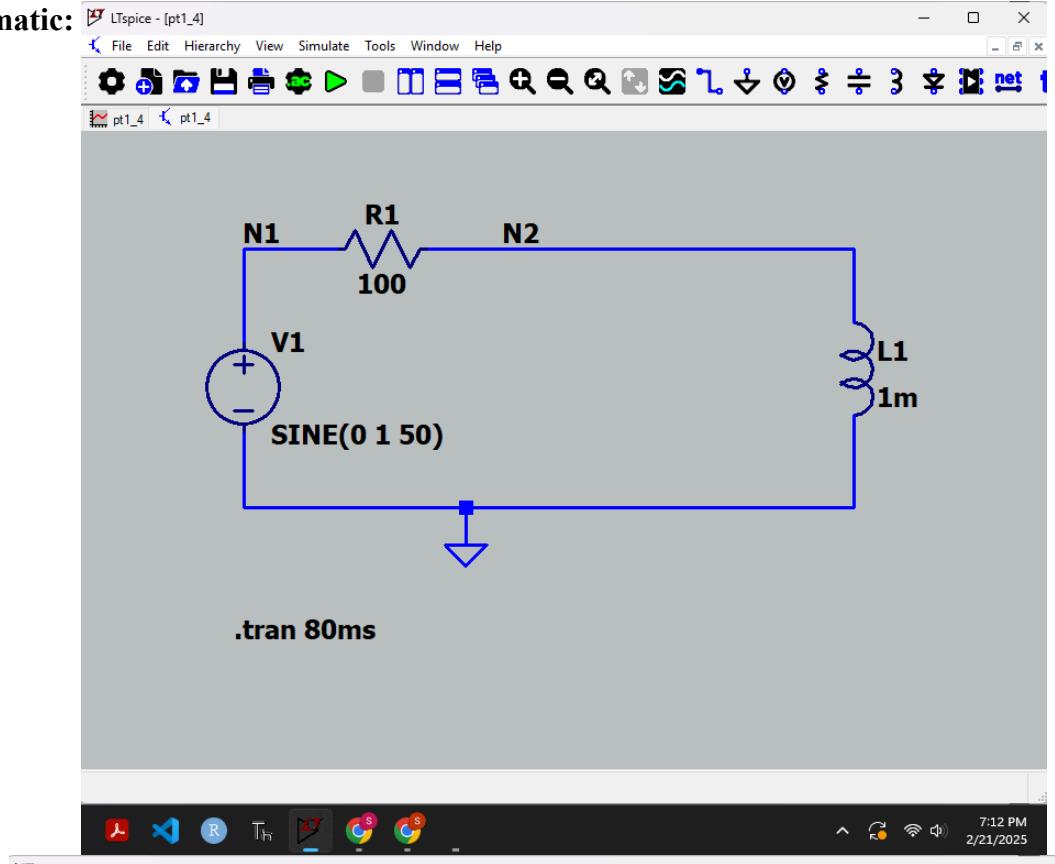

Screenshot of plot:

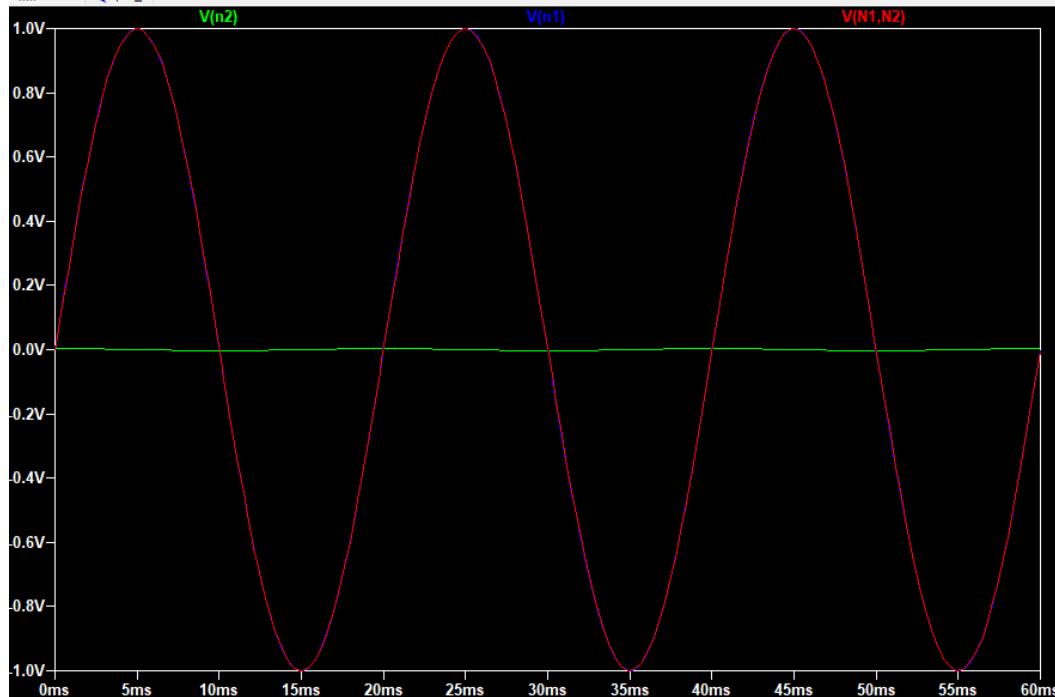

b) Magnitude difference between  $v_s(t)$  and  $v_L(t)$  = 0.9968 Volts

Phase difference between  $v_s(t)$  and  $v_L(t)$  = 90 Degrees

**Question 5 – RMS Calculations:****Show your work!****a) RMS value of a 2Vpp sine wave:**For a sine wave with peak-to-peak voltage  $V_{pp} = 2V$ , the amplitude is:

$$V_m = \frac{V_{pp}}{2} = \frac{2V}{2} = 1V$$

The voltage function is:

$$v(t) = V_m \sin(\omega t) = 1 \sin(\omega t)$$

Computing RMS:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T \sin^2(\omega t) dt}$$

Using the identity:

$$\int_0^T \sin^2(\omega t) dt = \frac{T}{2}$$

we get:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \times \frac{T}{2} \times V_m^2}$$

$$V_{\text{RMS}} = \frac{V_m}{\sqrt{2}} = \frac{1V}{\sqrt{2}} \approx 0.707V$$

**b) RMS value of a 2Vpp square wave:**For a square wave with constant amplitude  $V_m = 1V$ , the voltage function is:

$$v(t) = \pm V_m$$

Since the square of a constant is just itself:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T V_m^2 dt}$$

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \times (T \times V_m^2)}$$

$$V_{\text{RMS}} = V_m = 1V$$

**c) RMS value of a 2Vpp sawtooth wave:**

For a sawtooth wave that linearly ramps from  $-1V$  to  $+1V$ , we define:

$$v(t) = \frac{2V_m}{T}t - V_m$$

Since  $V_m = 1V$ , the function simplifies to:

$$v(t) = \frac{2}{T}t - 1$$

Computing RMS:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T \left( \frac{2}{T}t - 1 \right)^2 dt}$$

Expanding:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T \left( \frac{4}{T^2}t^2 - \frac{4}{T}t + 1 \right) dt}$$

Solving each integral using the reverse power rule and solving:

$$V_{\text{RMS}} = \sqrt{\frac{1}{T} \left[ \frac{4}{T^2} \times \frac{T^3}{3} - \frac{4}{T} \times \frac{T^2}{2} + T \right]} = \sqrt{\frac{1}{T} \left[ \frac{4T}{3} - 2T + T \right]}$$

$$V_{\text{RMS}} = \sqrt{\frac{4}{3} - 2 + 1}$$

$$V_{\text{RMS}} = \sqrt{\frac{1}{3}}$$

**Question 6 – Power Calculations:**

Show your work!

- a) Power of sine wave ( $\text{V}^2/\text{1K}$ ) averaged over time:
- b) Power of square wave ( $\text{V}^2/\text{1K}$ ) averaged over time:
- c) Power of sawtooth wave ( $\text{V}^2/\text{1K}$ ) averaged over time:

$$P_{\text{Sine Wave}} = \frac{(0.707V)^2}{1000} = 0.5 \text{ mW}$$

$$P_{\text{Square Wave}} = \frac{(1V)^2}{1000} = 1 \text{ mW}$$

$$P_{\text{Sawtooth Wave}} = \frac{(0.577V)^2}{1000} = 0.333 \text{ mW}$$

Comment on the relationship between the average power and the RMS value of the voltage (Provide a formula):

$$P = \frac{V_{\text{RMS}}^2}{R}$$

**Part 2 (10 pts): Hardware Lab Work**

1) a) Multimeter reading of a 2Vpp sine wave: \_\_\_\_\_ 0.5 \_\_\_\_\_ V

b) Multimeter reading of a 2Vpp square wave: \_\_\_\_\_ 0.8 \_\_\_\_\_ V

c) Multimeter reading of a 2Vpp sawtooth wave: \_\_\_\_\_ 0.3 \_\_\_\_\_ V


d) Based on your measurements, does the multimeter provide peak-to-peak voltages or RMS voltages?

RMS voltages

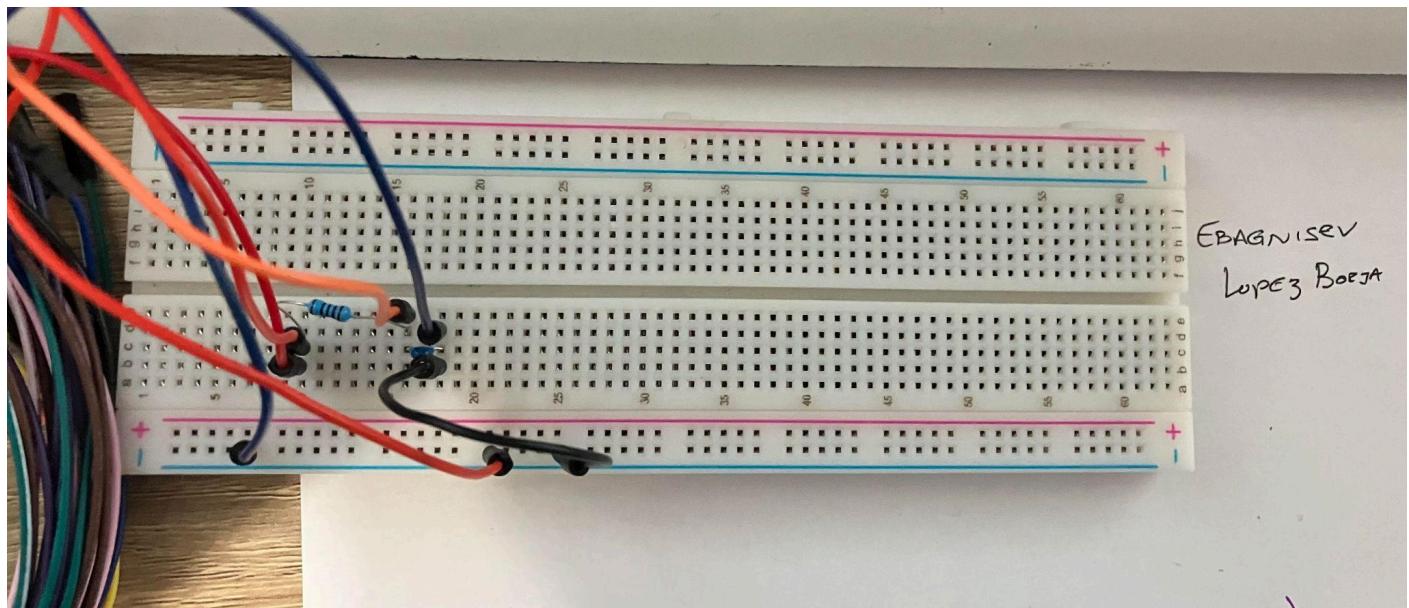**2) Hardware RC circuit – Pulse Source**


Build RC circuit on hardware and connect both channels of oscilloscope

Include a photo of your hardware circuit here (Have a look at an example photo at the end of this document):



**Using your oscilloscope, plot  $v_s(t)$  and  $v_c(t)$ ). Make sure both waves are displayed on the same figure and the numbers are readable in the screenshot:**

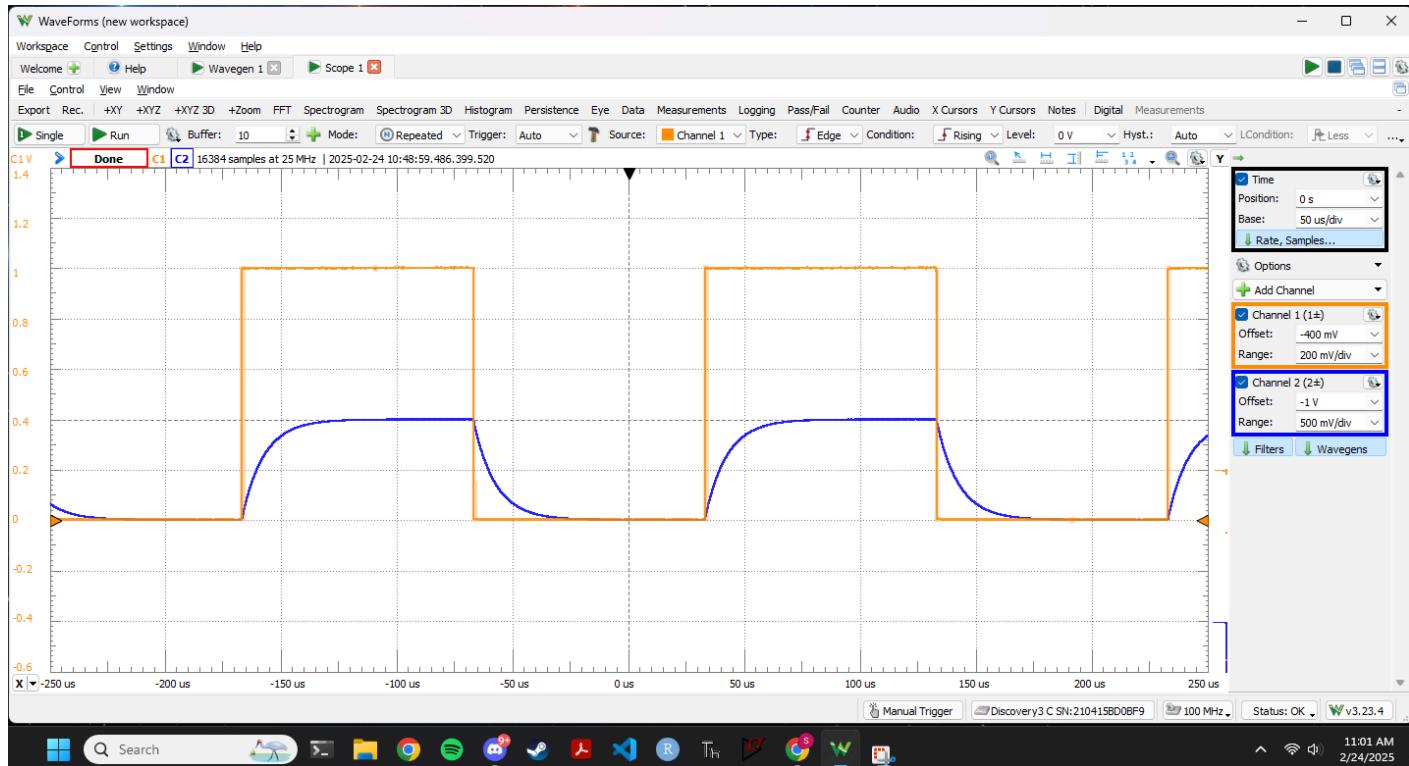**Screenshot of Oscilloscope Plot - Make sure that your computer's date and time are showing up in your screenshot:**




### 3) Hardware – RC Circuit – Sine Wave:

Change the voltage source (waveform W1 on your Analog Discovery kit) to a sine wave with the parameters as indicated in the manual.

**Using your oscilloscope, plot  $v_s(t)$  and  $v_c(t)$ ). Make sure both waves are displayed on the same figure and the numbers are readable in the screenshot:**

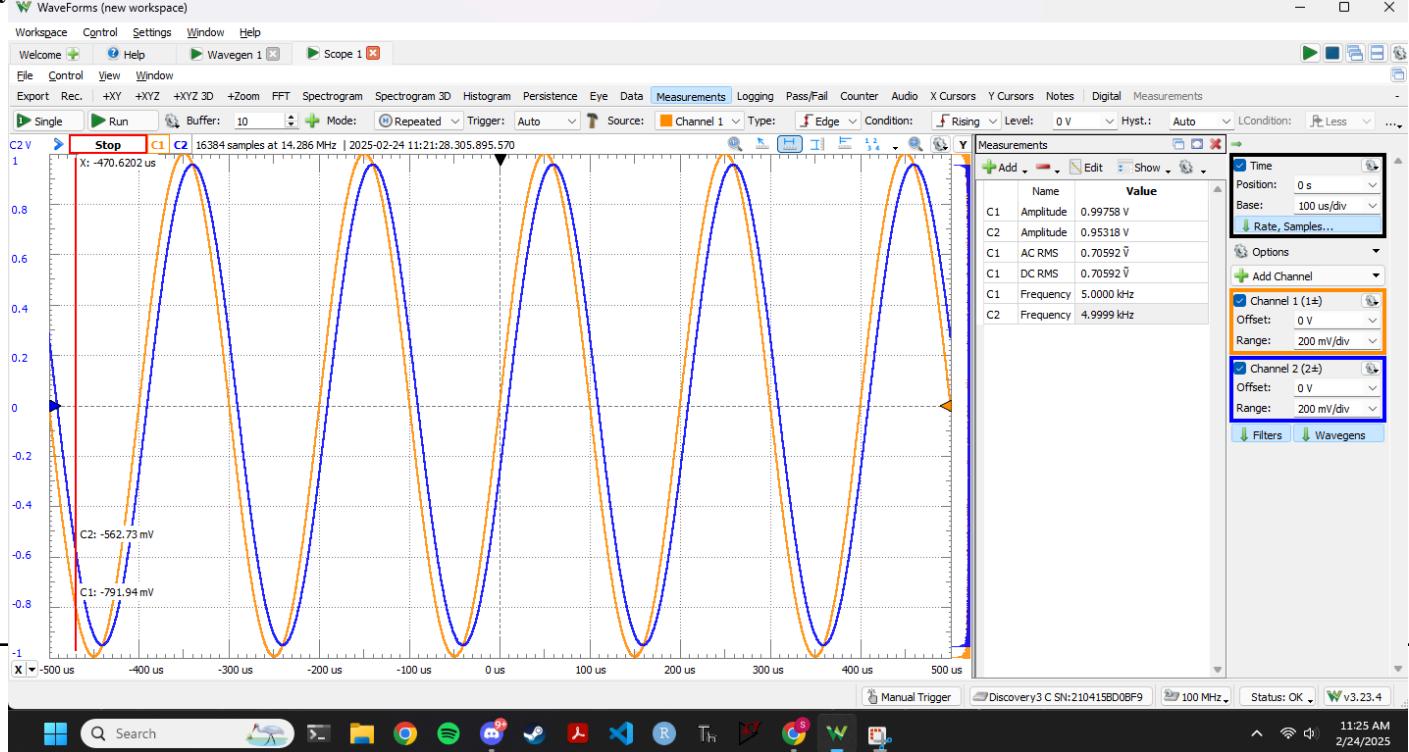**Screenshot of Oscilloscope Plot - Make sure that your computer's date and time are showing up in your screenshot:**




Provide the following from the oscilloscope plot of your RC circuit:

- a) The magnitude of the voltage across the capacitor: 0.95318 V
- b) The RMS of the voltage from the source: 0.70592 V
- c) The phase difference, in degrees, between the source and cap voltage: 17.64 Degrees
- d) The capacitor voltage is lagging the source voltage  
leading or lagging

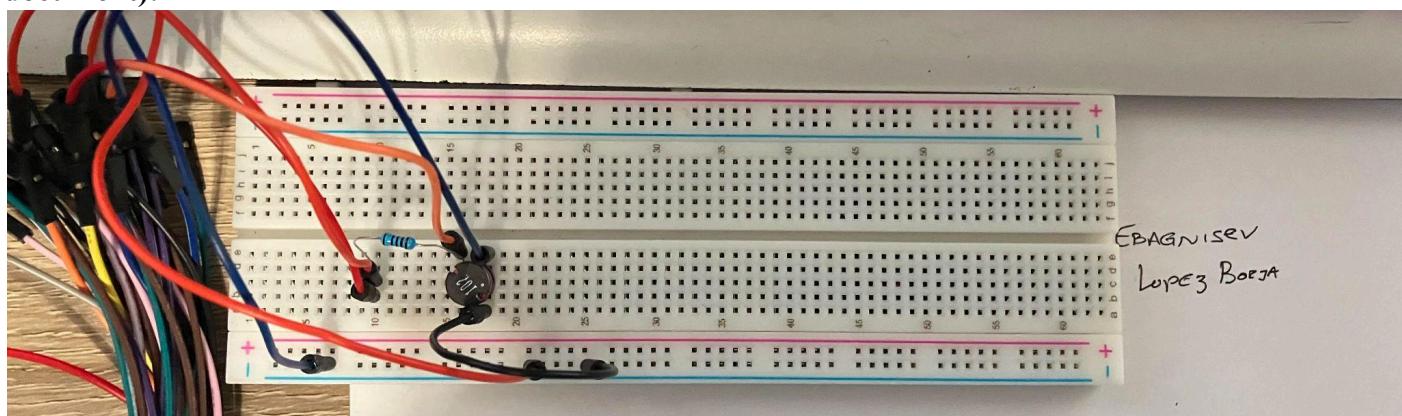
4) Hardware - RL Circuit – Sine Wave:

Include a photo of your hardware circuit here (Have a look at an example photo at the end of this document):



Using your oscilloscope, plot  $v_s(t)$  and  $v_L(t)$ . Make sure both waves are displayed on the same figure and the numbers are readable in the screenshot:

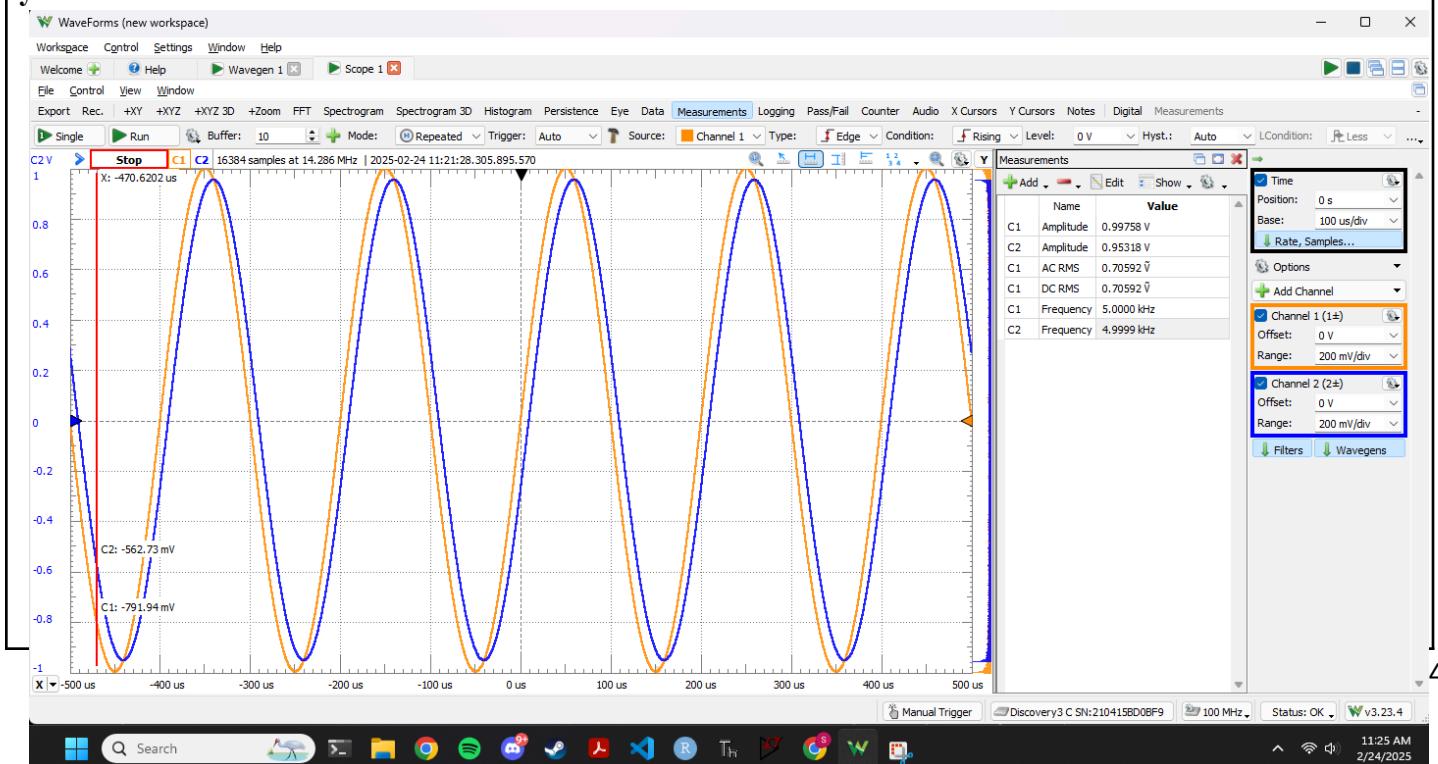Screenshot of Oscilloscope Plot - Make sure that your computer's date and time are showing up in your screenshot:



Provide the following from the oscilloscope plot of your RL circuit:

a) The magnitude of the voltage across the inductor:

24.991 mV

b) The RMS of the voltage from the source:

0.70312 V


c) The phase difference, in degrees, between the source and inductor voltage: 3.906 Degrees

d) The inductor voltage is leading the source voltage  
leading or lagging
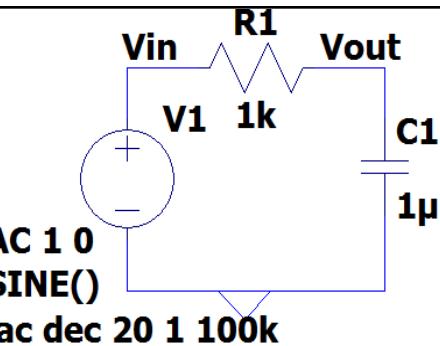
### Part 3: Extra Credit (10 pts) - Bode Plots


Create bode plots of the shown RC circuit (*magnitude in dB, phase in degrees*) and attach an image of your plot here.

Make sure the numbers are readable in the photo. You can depend on LTSpice as explained in the manual above or use the Analog Discovery 2 kit as explained in the following video [https://youtu.be/31tq\\_A\\_2TcY](https://youtu.be/31tq_A_2TcY). Circuit connections are explained at min 4:16)




Bode plot (including magnitude and phase plots):

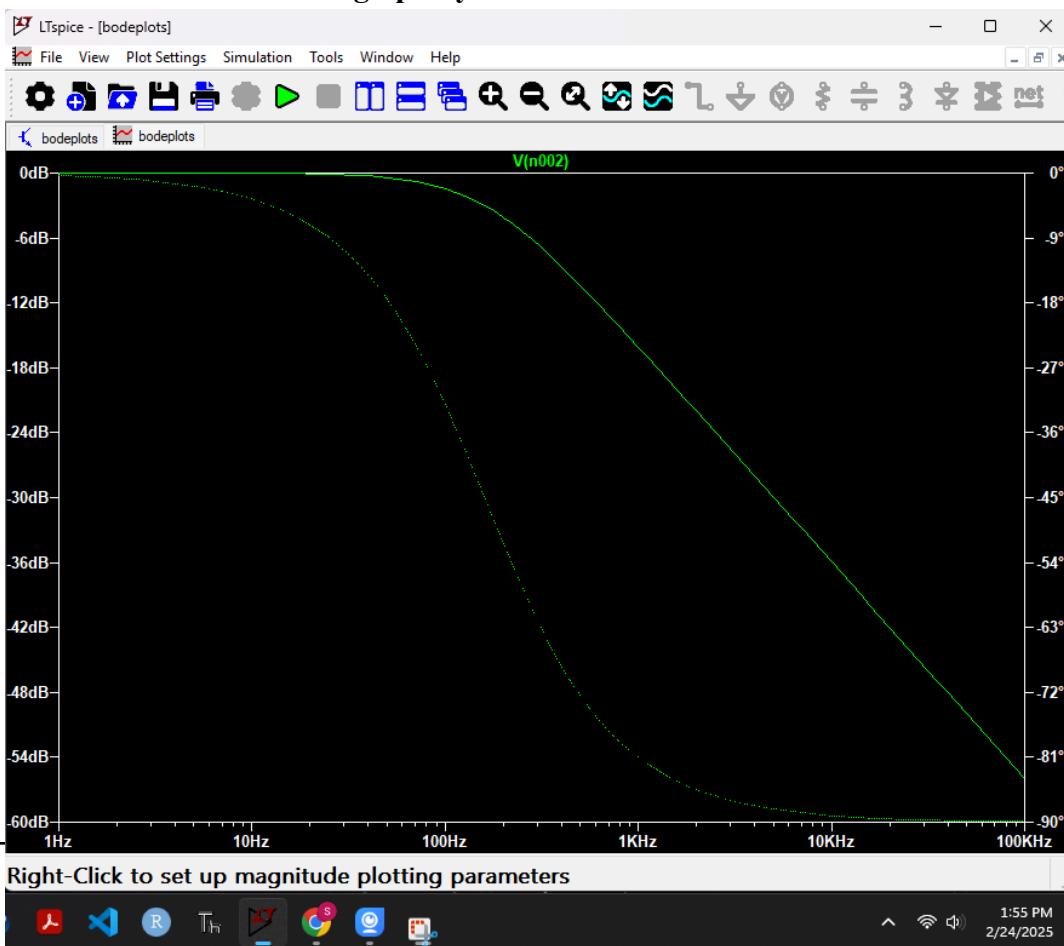Screenshot of Oscilloscope Plot - Make sure that your computer's date and time are showing up in your screenshot:



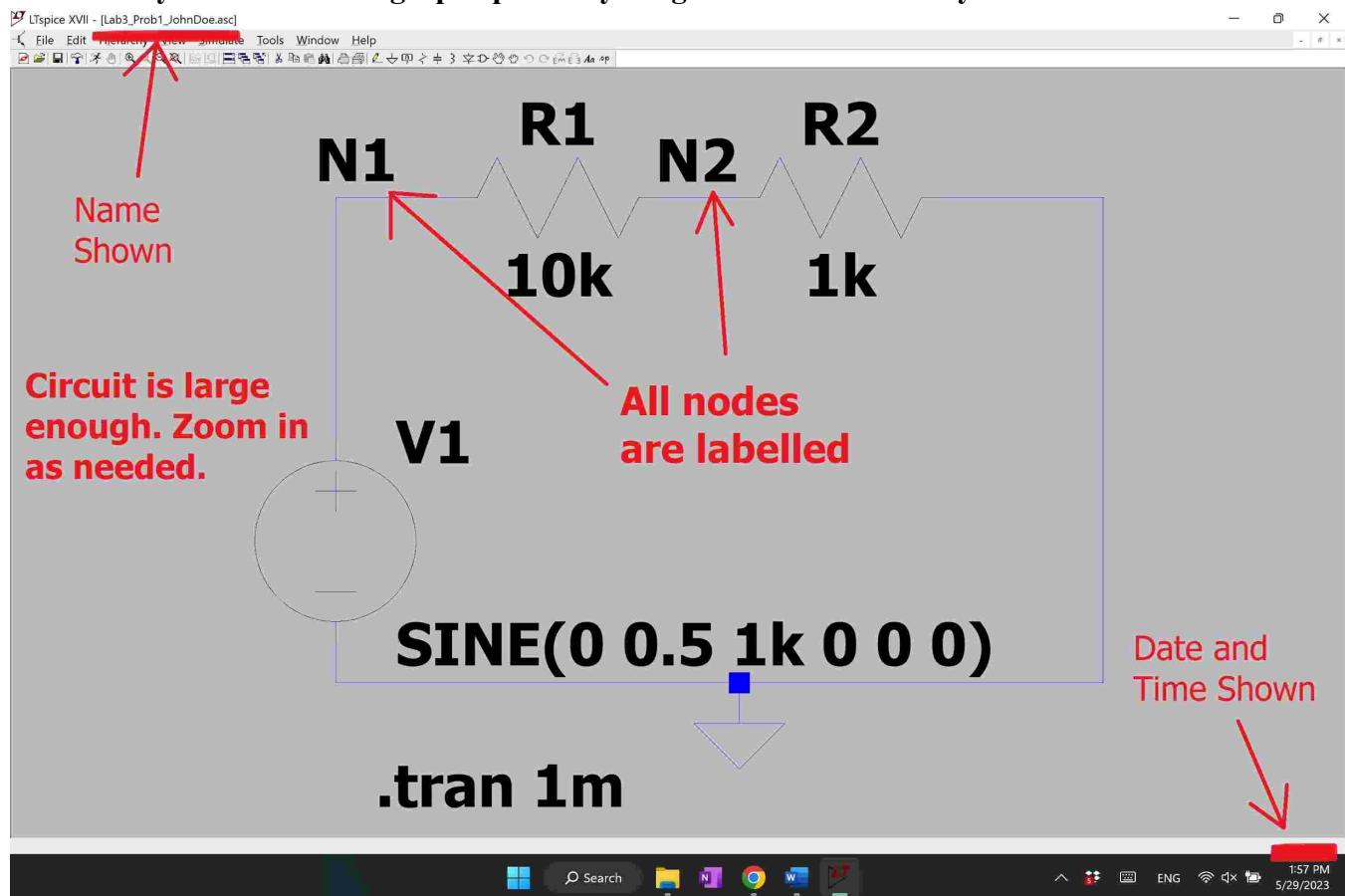**LTS spice Screenshot Example (Note your name, date and time, readable circuit, and labelled nodes – screenshots might vary based on the operating system you are using) – This applies to screenshots of circuits only. Screenshots of graphs/plots/anything else can include only the date and time.**



**Hardware Image Example. Note your name:**

- 1- on a piece of paper; OR
- 2- typed electronically (must be typed on the breadboard WITHOUT any “text background”.  
Breadboard must show up in the background of your name.)

